

# COMS12200

# Introduction to

# Computer Architecture

**Dr. Cian O'Donnell**  
*[cian.odonnell@bristol.ac.uk](mailto:cian.odonnell@bristol.ac.uk)*

**Topic 5: State machines and decoding**

# Topics

1. Data, Control and Instructions
2. Memory
3. Execution cycle
4. Processor control flow
5. State machines and decoding
6. Machine types
7. Memory paradigms

# 4. Processor control flow

## Summary from previous lecture


- We looked at **branching**
- And its use in:
  - `for` loops
  - `if/else` statements
  - calling sub-routines (functions)
- How they are implemented in hardware using the **link register** and the **stack**.

# Topics

1. Data, Control and Instructions
2. Memory
3. Execution cycle
4. Processor control flow
5. State machines and decoding
6. Machine types
7. Memory paradigms
 
# State machine recap

- A state machine is one with a finite set of defined states.
- Transitions are made between states.
- Transitions can be gated or ungated.




# State machine recap

Each state is uniquely labeled and transitions can also be expressed in a table.

Current state	Next state	Condition
s0	s1	Always
s1	s2	Always
s2	s0	Always

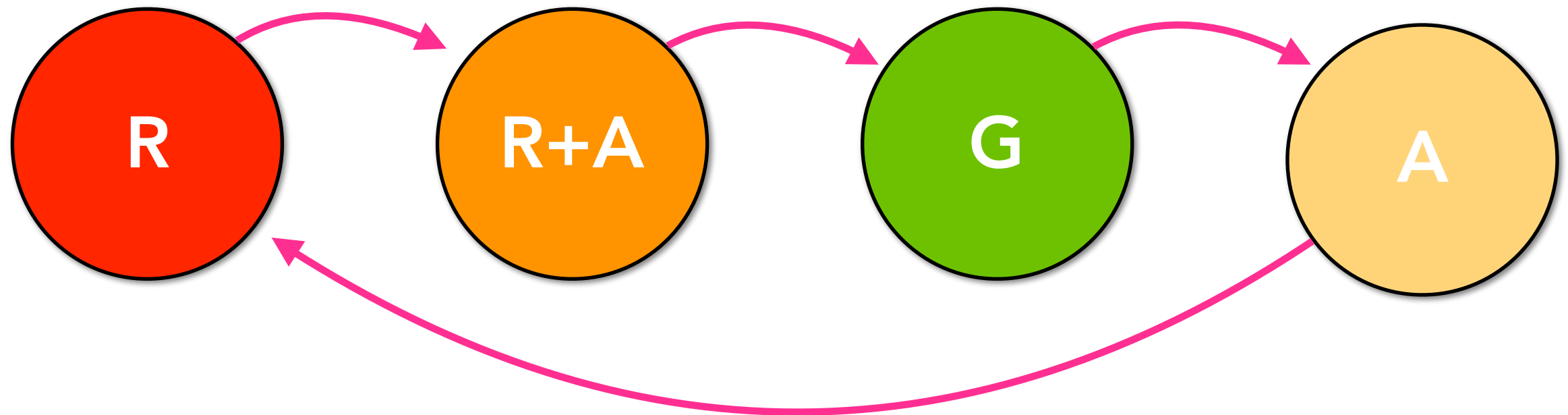
# Traffic lights

A traffic light is a **useful** state machine with four states.



# The simplest 4-state machine

2 bits =  $2^2 = 4$  states

 




Decoding states
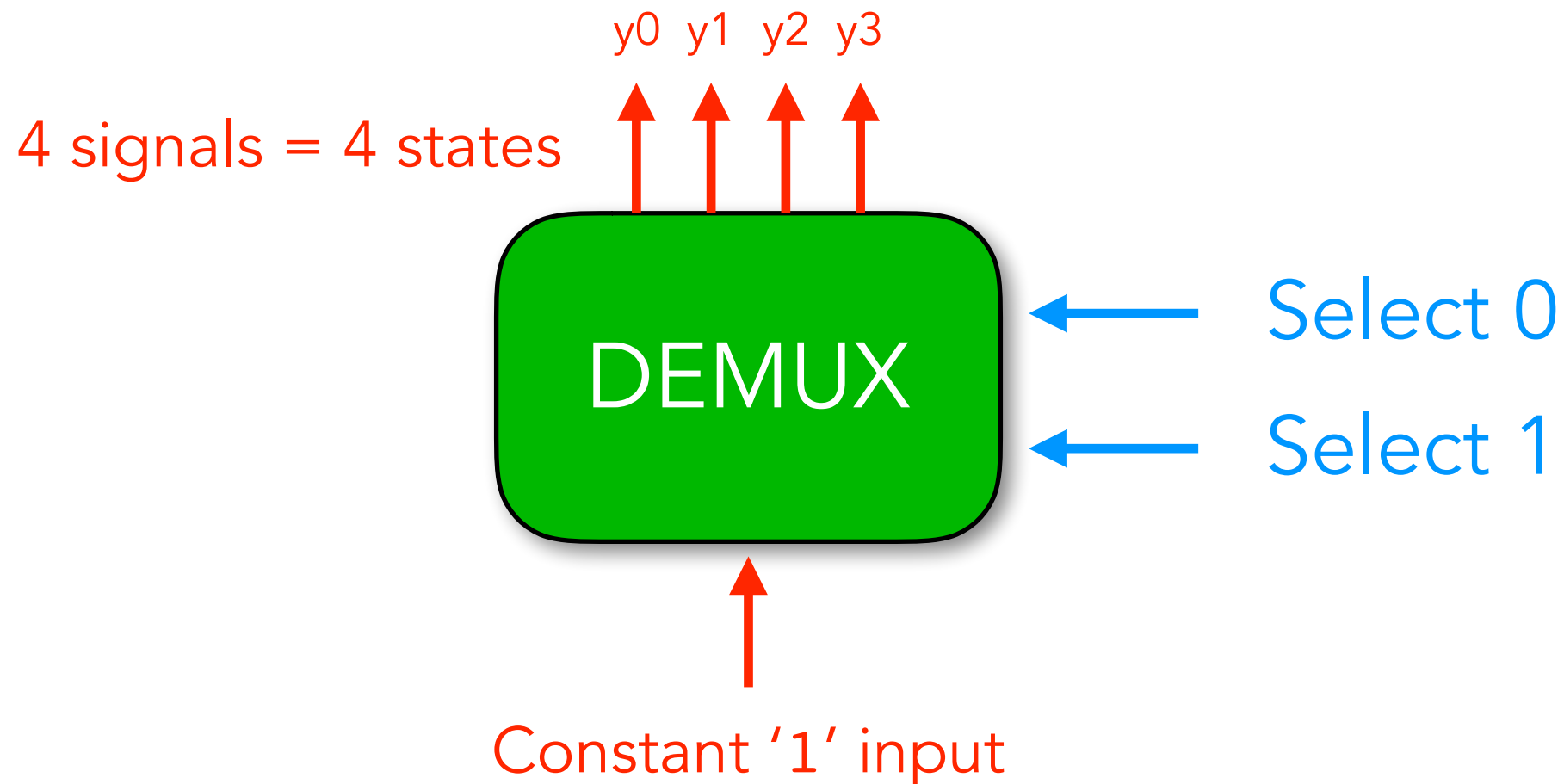
# A four state decoder

**Q:** How can we uniquely decode a state from our simple machine?

**A:** A demultiplexor solves the problem.



# From states to lights

How do we convert the decoder outputs to the **R**, **A**, **G** values for a simple traffic light?

# From states to lights

- Observe that each of the decoder outputs has produced a minterm.
- Each minterm is unique and can be manipulated via boolean logic.
- Typically, we will combine minterms via logical gates to obtain a compound output (e.g. Red light from R and R/A minterms).


Variable control signals

# Why vary control?

- In your labs so far, you have made static systems: ones that do the same task again and again (and again)
- To change their behaviour, you have used switches.
- This is great for simple tasks, but we'd really like to be **hands off** when computing more complex things.
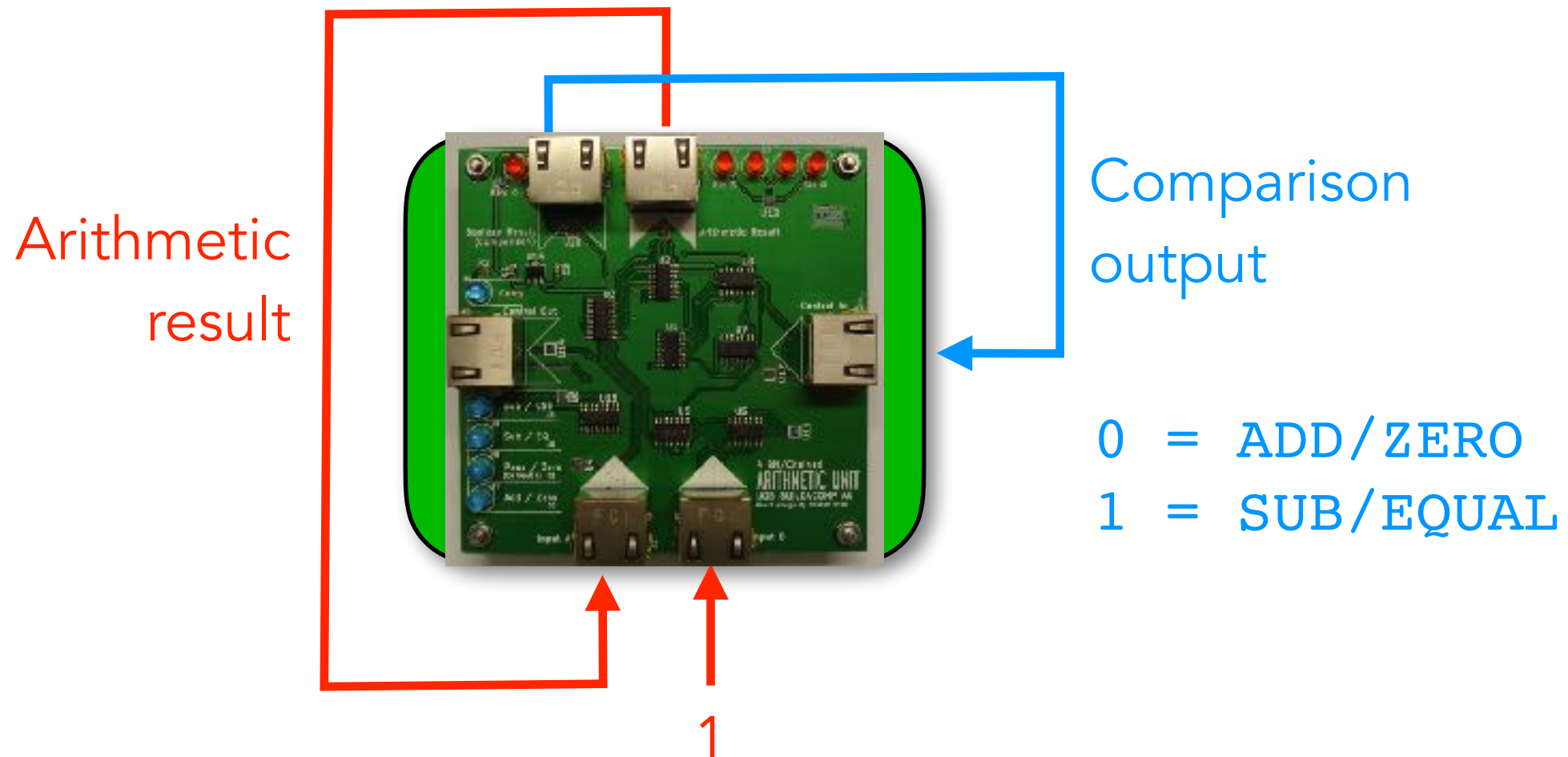
# Supporting variable control

Here's a very simple example of how we could vary control to do something useful:



# Feedback

- Feedback was the key thing that made the previous example do something interesting.
- Feedback is when a previous output from a system is used to alter its current behaviour:


$$S_{n+1} = f(S_n, \text{inputs})$$




# Feedback to change operations

- We can use feedback to alter both the data inputs and/or the function of a unit.
- There are several useful implementation methodologies.
- Now we'll look at one simple one

# Changing the data inputs

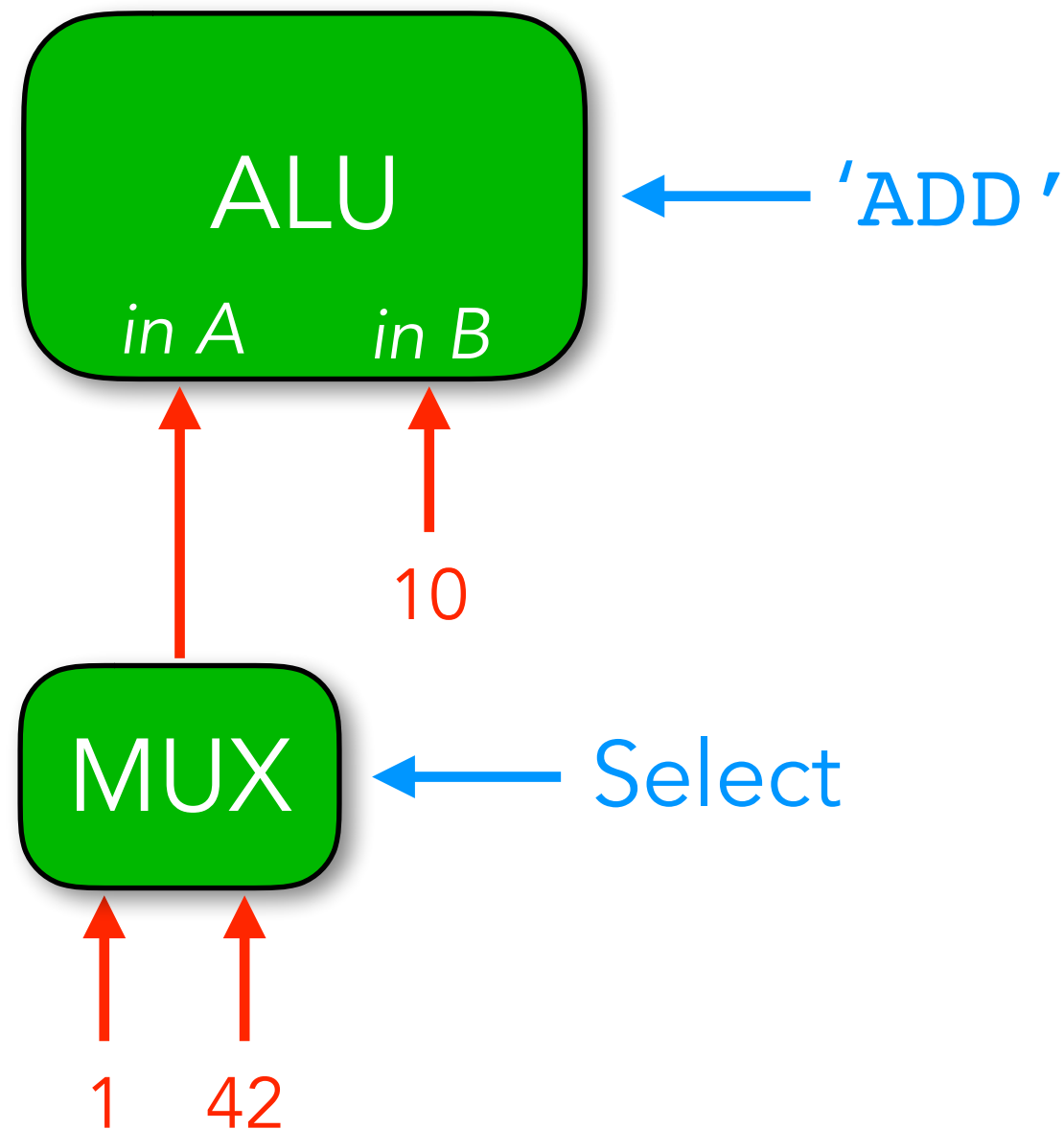

# Changing the control inputs

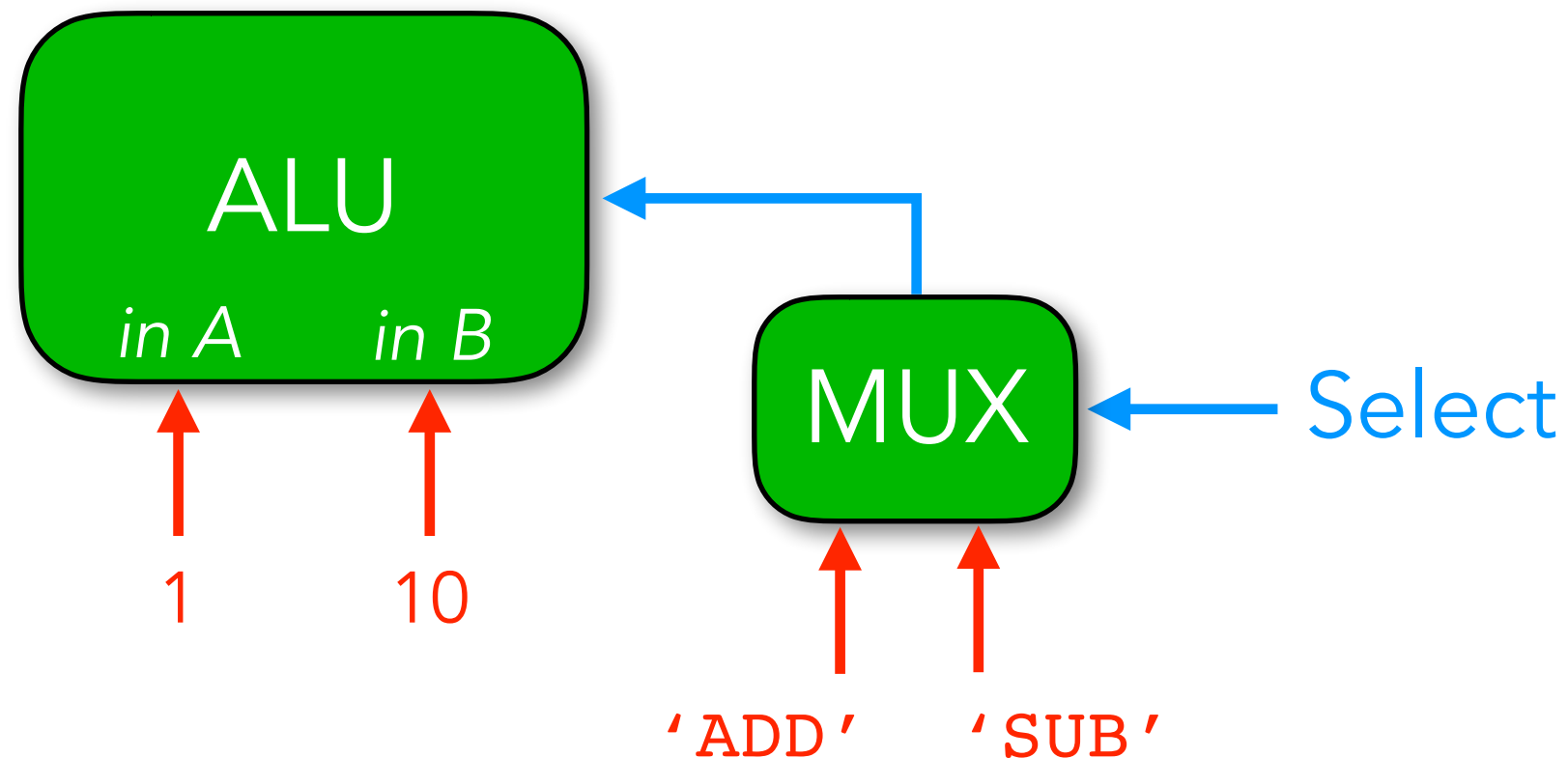

# Selecting the input

- Where do the select signals come from?
  - They could come from instructions
  - Instructions will dictate behaviour
- They could come from feedback
  - Data values will dictate behaviour

# Notes

Here are three useful guidelines when creating control flow for state machines:

1. **MUXs** are useful for selecting inputs
2. **DEMUXs** are useful for decoding outputs
3. **OR gates** are useful for combining states and producing feedback signals.

# Week 11 Labs

## This week you will:

- Build a series of different **traffic lights** circuits using ideas from today's lecture (state machines and decoding).