

Intro. to Computer Architecture

Daniel Page

Department of Computer Science,
University Of Bristol,
Merchant Venturers Building,
Woodland Road,
Bristol, BS8 1UB. UK.
(csdsp@bristol.ac.uk)

January 9, 2018

Keep in mind there are *two* PDFs available (of which this is the latter):

1. a PDF of examinable material used as lecture slides, and
2. a PDF of non-examinable, extra material:
 - ▶ the associated notes page may be pre-populated with extra, written explanation of material covered in lecture(s), plus
 - ▶ anything with a “grey’ed out” header/footer represents extra material which is useful and/or interesting but out of scope (and hence not covered).

Notes:

Notes:

Continued from last lecture ...

Notes:

“Building Block” Components (1) Choice

- ▶ Just two building blocks can support most forms of choice:
 1. a **multiplexer**
 - ▶ has m inputs,
 - ▶ has 1 output,
 - ▶ uses a $(\lceil \log_2(m) \rceil)$ -bit control signal input to choose which input is connected to the output,
 - while
 2. a **demultiplexer**
 - ▶ has 1 input,
 - ▶ has m outputs,
 - ▶ uses a $(\lceil \log_2(m) \rceil)$ -bit control signal input to choose which output is connected to the input,
- noting that
 - ▶ the input(s) and output(s) are n -bit, but clearly must match up,
 - ▶ the connection made is continuous, since both components are combinatorial.

Notes:

- As an analogy, the C switch statement

Listing

```
1 switch( c ) {
2   case 0 : r = w; break;
3   case 1 : r = x; break;
4   case 2 : r = y; break;
5   case 3 : r = z; break;
6 }
```

acts similarly to a 4-input multiplexer.

- Likewise,

Listing


```
1 switch( c ) {
2   case 0 : r0 = x; break;
3   case 1 : r1 = x; break;
4   case 2 : r2 = x; break;
5   case 3 : r3 = x; break;
6 }
```

acts similarly to a 4-output demultiplexer.

Notes:

Definition

 The behaviour of a 2-input, 1-bit multiplexer component




is described by the truth table

MUX2				
<i>c</i>	<i>x</i>	<i>y</i>	<i>r</i>	
0	0	?	0	
0	1	?	1	
1	?	0	0	
1	?	1	1	

which can be used to derive the following implementation:

$$r = (\neg c \wedge x) \vee (c \wedge y)$$


Circuit

 

Notes:

Definition

 The behaviour of a **2-output, 1-bit demultiplexer** component




is described by the truth table

DEMUX2			
c	x	r ₁	r ₀
0	0	?	0
0	1	?	1
1	0	0	?
1	1	1	?

which can be used to derive the following implementation:

$$\begin{aligned} r_0 &= \neg c \wedge x \\ r_1 &= c \wedge x \end{aligned}$$


Circuit

 

Notes:


An Aside: Applying our design patterns

 Circuit (2-input, 4-bit multiplexer via isolated replication)



Notes:

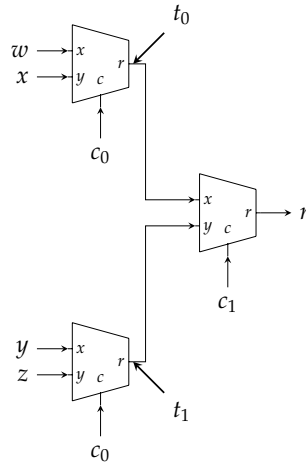Circuit (4-input, 1-bit multiplexer via cascaded replication)



Notes:

“Building Block” Components (7)

Addition

- ▶ Just two building blocks can support most forms of arithmetic:

1. a **half-adder**

- ▶ has 2 inputs: x and y ,
- ▶ computes the 2-bit result $x + y$,
- ▶ has 2 outputs: a sum s , and a carry-out co (which are the LSB and MSB of result),

while

2. a **full-adder**

- ▶ has 3 inputs: x and y plus a carry-in ci ,
- ▶ computes the 2-bit result $x + y + ci$,
- ▶ has 2 outputs: a sum s , and a carry-out co (which are the LSB and MSB of result),

where all inputs and outputs are 1-bit.

Notes:

Definition

The behaviour of a **half-adder** component




is described by the truth table

HALF-ADDER			
x	y	co	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

which can be used to derive the following implementation:

$$\begin{aligned} co &= x \wedge y \\ s &= x \oplus y \end{aligned}$$

Circuit

 

Notes:

Definition

The behaviour of a **full-adder** component




is described by the truth table

FULL-ADDER				
ci	x	y	co	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

which can be used to derive the following implementation:


$$\begin{aligned} co &= (x \wedge y) \vee (x \wedge ci) \vee (y \wedge ci) \\ &= (x \wedge y) \vee ((x \oplus y) \wedge ci) \\ s &= x \oplus y \oplus ci \end{aligned}$$

Circuit

 

Notes:

Circuit (n -bit addition)

 

Notes:

“Building Block” Components (11) Comparison

- Just two building blocks can support most forms of comparison:

1. an **equality comparator**

- has 2 inputs x and y ,
- computes the 1 output as

$$r = \begin{cases} 1 & \text{if } x = y \\ 0 & \text{otherwise} \end{cases}$$

while

2. a **less-than comparator**

- has 2 inputs x and y ,
- computes the 1 output as

$$r = \begin{cases} 1 & \text{if } x < y \\ 0 & \text{otherwise} \end{cases}$$

where all inputs and outputs are 1-bit.

Notes:

Definition

The behaviour of an **equality comparator** component




is described by the truth table

EQUAL		
x	y	r
0	0	1
0	1	0
1	0	0
1	1	1

which can be used to derive the following implementation:

$$r = \neg(x \oplus y)$$

Circuit

 

Notes:

Definition

The behaviour of a **less-than comparator** component




is described by the truth table

LESS-THAN		
x	y	r
0	0	0
0	1	1
1	0	0
1	1	0


which can be used to derive the following implementation:

$$r = \neg x \wedge y$$


Circuit

 

Notes:

 


Notes:

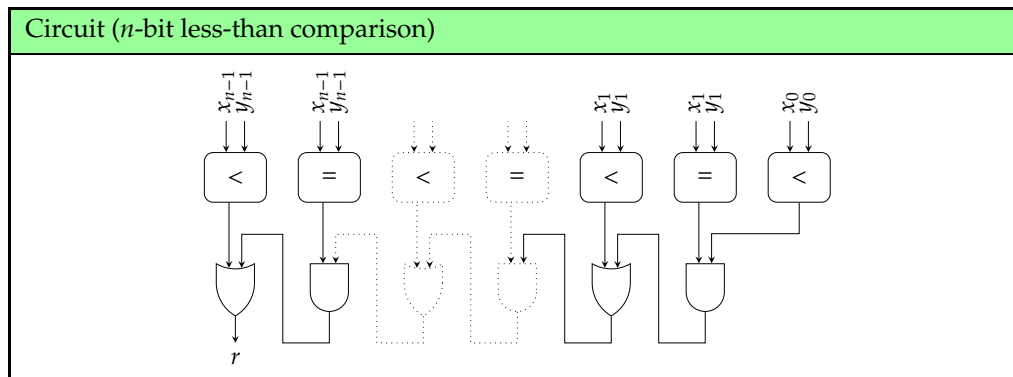

Notes:

 - Informally at least, **encoder** and **decoder** components can be viewed as *translators*



or, more formally,

- an n -to- m encoder translates an n -bit input into some m -bit code word, and
- an m -to- n decoder translates an m -bit code word back into the same n -bit output

where if only one output (resp. input) is allowed to be 1 at a time, we call it a **one-of-many** encoder (resp. decoder).

Notes:

- A *general* building block is impossible since it depends on the scheme for encoding/decoding: consider an [example](#) st.
 - to encode, take n inputs, say x_i for $0 \leq i < n$, and produce a unsigned integer x' that determines which $x_i = 1$,
 - to decode, take x' and set the right $x_i = 1$where for all $j \neq i$, $x'_j = 0$ (so both are one-of-many).

Notes:

Definition (example encoder)


The example encoder is described by the truth table

ENC-4-TO-2					
x_3	x_2	x_1	x_0	x'_1	x'_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

which can be used to derive the following implementation:

$$\begin{aligned}x'_0 &= x_1 \vee x_3 \\x'_1 &= x_2 \vee x_3\end{aligned}$$

Circuit (example encoder)

 

Notes:

Definition (example decoder)


The example decoder is described by the truth table

DEC-2-TO-4					
x'_1	x'_0	x_3	x_2	x_1	x_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

which can be used to derive the following implementation:

$$\begin{aligned}x_0 &= \neg x'_0 \wedge \neg x'_1 \\x_1 &= x'_0 \wedge \neg x'_1 \\x_2 &= \neg x'_0 \wedge x'_1 \\x_3 &= x'_0 \wedge x'_1\end{aligned}$$

Circuit (example decoder)

 

Notes:

- **Problem:** if we break the rules and set both $x_1 = 1$ and $x_2 = 1$, the encoder fails by producing

$$\begin{array}{rclclcl} x'_0 & = & x_1 \vee x_3 & = & 1 \\ x'_1 & = & x_2 \vee x_3 & = & 1 \end{array}$$

as the result.

- **Solution:** consider a **priority** encoder, where one input is given priority (or preference) over another.

Notes:

Notes:

Example

Imagine we want to give x_j priority over each x_k for $j > k$, so x_2 over x_1 and x_0 for example:

PRIORITYENC-4-TO-2					
x_3	x_2	x_1	x_0	x'_1	x'_0
0	0	0	1	0	0
0	0	1	?	0	1
0	1	?	?	1	0
1	?	?	?	1	1

Now, although potentially $x_0 = 1$ or $x_1 = 1$ the output gives priority to x_2 : as long as $x_2 = 1$ and $x_3 = 0$, the output will be $x'_0 = 0$ and $x'_1 = 1$ irrespective of x_0 and x_1 .

Conclusions

► Take away points:

1. There are a *huge* number of challenges, even with (relatively) simple problems, e.g.,
 - how do we describe what the design should do?
 - how do we structure the design?
 - what sort of standard cell library do we use?
 - do we aim for the fewest gates?
 - do we aim for shortest critical path?
 - how do we cope with propagation delay and fan-out?
 - ...
2. The three themes we've covered, i.e.,
 - high-level design patterns,
 - low-level, mechanical derivation and optimisation of Boolean expressions,
 - building-block components,

allows us to address such challenges: in combination, they support development of effective (combinatorial) design and implementation.

3. In many cases, use of appropriate **Electronic Design Automation (EDA)** tools can provide (semi-)automatic solutions.

Notes:

Additional Reading

- *Wikipedia: Combinational logic*. URL: http://en.wikipedia.org/wiki/Combinational_logic.
- D. Page. “Chapter 2: Basics of digital logic”. In: *A Practical Introduction to Computer Architecture*. 1st ed. Springer-Verlag, 2009.
- W. Stallings. “Chapter 11: Digital logic”. In: *Computer Organisation and Architecture*. 9th ed. Prentice-Hall, 2013.
- A.S. Tanenbaum and T. Austin. “Section 3.2.2: Combinatorial circuits”. In: *Structured Computer Organisation*. 6th ed. Prentice-Hall, 2012.

Notes:

References

- [1] [Wikipedia: Combinational logic](http://en.wikipedia.org/wiki/Combinational_logic). URL: http://en.wikipedia.org/wiki/Combinational_logic (see p. 51).
- [2] D. Page. “Chapter 2: Basics of digital logic”. In: *A Practical Introduction to Computer Architecture*. 1st ed. Springer-Verlag, 2009 (see p. 51).
- [3] W. Stallings. “Chapter 11: Digital logic”. In: *Computer Organisation and Architecture*. 9th ed. Prentice-Hall, 2013 (see p. 51).
- [4] A.S. Tanenbaum and T. Austin. “Section 3.2.2: Combinatorial circuits”. In: *Structured Computer Organisation*. 6th ed. Prentice-Hall, 2012 (see p. 51).

Notes: