

Intro. to Computer Architecture

Daniel Page

Department of Computer Science,
University Of Bristol,
Merchant Venturers Building,
Woodland Road,
Bristol, BS8 1UB. UK.
(csdsp@bristol.ac.uk)

January 9, 2018

Keep in mind there are *two* PDFs available (of which this is the latter):

1. a PDF of examinable material used as lecture slides, and
2. a PDF of non-examinable, extra material:
 - ▶ the associated notes page may be pre-populated with extra, written explanation of material covered in lecture(s), plus
 - ▶ anything with a “grey’ed out” header/footer represents extra material which is useful and/or interesting but out of scope (and hence not covered).

Notes:

Notes:

► Recap:

Definition

A (deterministic) **Finite State Machine (FSM)** is a tuple

$$C = (S, s, A, \Sigma, \Gamma, \delta, \omega)$$

including

1. S , a finite set of **states** that includes a **start state** $s \in S$,
2. $A \subseteq S$, a finite set of **accepting states**,
3. an **input alphabet** Σ and an **output alphabet** Γ ,
4. a **transition function**

$$\delta : S \times \Sigma \rightarrow S$$

and

5. an **output function**

$$\omega : S \rightarrow \Gamma$$

in the case of a **Moore FSM**, or

$$\omega : S \times \Sigma \rightarrow \Gamma$$


in the case of a **Mealy FSM**,

noting an **empty** input denoted ϵ allows a transition that can *always* occur.

Notes:

FSMs in Hardware (1)

Algorithm (latch version)

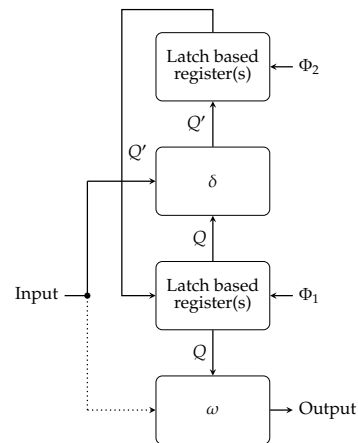


► Note that

1. the state is retained in a register (i.e., a group of latches, resp. flip-flops),
2. δ and ω are simply combinatorial logic,
3. within the current clock cycle
 - 3.1 ω computes the output from the current state and input, and
 - 3.2 δ computes the next state from the current state and input,
4. the next state is latched by an appropriate feature (i.e., level, resp. edge) in the clock

i.e., this is a framework for a *computer* we can *build*!

Notes:

Algorithm (flip-flop version)

 


► Note that

1. the state is retained in a register (i.e., a group of latches, resp. flip-flops),
2. δ and ω are simply combinatorial logic,
3. within the current clock cycle
 - 3.1 ω computes the output from the current state and input, and
 - 3.2 δ computes the next state from the current state and input,
4. the next state is latched by an appropriate feature (i.e., level, resp. edge) in the clock

i.e., this is a framework for a *computer* we can *build*!


Notes:

FSMs in Hardware (3)

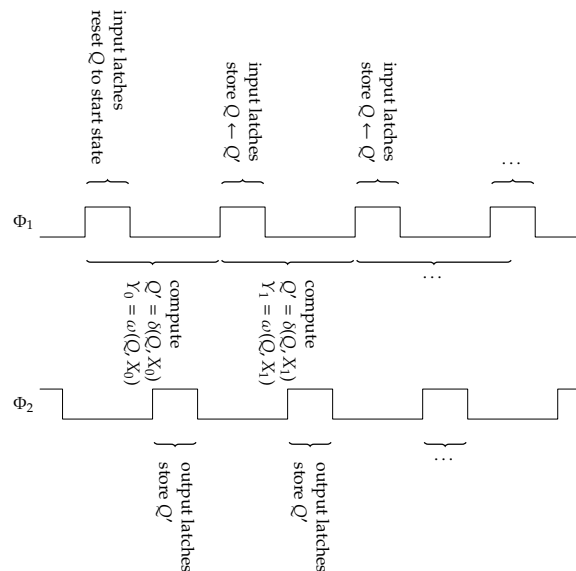Example (latch version: given input $X = \langle X_0, X_1, \dots \rangle$ and output $Y = \langle Y_0, Y_1, \dots \rangle$)

Notes:

 
Example (flip-flop version: given input $X = \langle X_0, X_1, \dots \rangle$ and output $Y = \langle Y_0, Y_1, \dots \rangle$)



Notes:

FSMs in Hardware (5)

Circuit (latch version)

 


- ▶ This *should* sound familiar:
 - ▶ 2^n states, labelled S_0 through S_{2^n-1} ; state S_i represented as (unsigned) n -bit integer i ,
 - ▶ the start state is $s = S_0$ and there are no accepting states (so $A = \emptyset$),
 - ▶ the δ function is

$$Q' \leftarrow \delta(Q, rst) = \begin{cases} Q + 1 & (\text{mod } 2^n) & \text{if } rst = 0 \\ 0 & & \text{if } rst = 1 \end{cases}$$

- ▶ the ω function is $r \leftarrow \omega(Q) = Q$.

Notes:

Circuit (flip-flop version)

 

► This *should* sound familiar:

- 2^n states, labelled S_0 through S_{2^n-1} ; state S_i represented as (unsigned) n -bit integer i ,
- the start state is $s = S_0$ and there are no accepting states (so $A = \emptyset$),
- the δ function is

$$Q' \leftarrow \delta(Q, rst) = \begin{cases} Q + 1 \pmod{2^n} & \text{if } rst = 0 \\ 0 & \text{if } rst = 1 \end{cases}$$

- the ω function is $r \leftarrow \omega(Q) = Q$.

Notes:

FSMs in Hardware (7)

- To use the framework to solve a concrete problem, we follow a (fairly) standard sequence of steps

Algorithm

1. Count the number of states required, and give each state an abstract label.
2. Describe the state transition and output functions using a tabular or diagrammatic approach.
3. Perform state assignment, i.e., decide how concrete values will represent the abstract labels, allocating appropriate register(s) to hold the state.
4. Express the functions δ and ω as (optimised) Boolean expressions, i.e., combinatorial logic.
5. Place the registers and combinatorial logic into the framework.

noting that it's common to

- include a **reset** input that (re)initialises the FSM into the start state,
- replace the accepting state(s) with an **idle** or **error** state since "halting" doesn't make sense in hardware, and
- use the FSM to control an associated data-path using the outputs, rather than (necessarily) solve some problem outright.

Notes:

- ▶ The fact we do state assignment late on in the process is intentional; it allows us to optimise the representation based on what we do with it.

1. A **binary encoding** represents the i -th of n states as a $(\lceil \log_2(n) \rceil)$ -bit unsigned integer i , e.g.,

$$\begin{aligned} S_0 &\mapsto \langle 0, 0, 0 \rangle \\ S_1 &\mapsto \langle 1, 0, 0 \rangle \\ S_2 &\mapsto \langle 0, 1, 0 \rangle \\ S_3 &\mapsto \langle 1, 1, 0 \rangle \\ S_4 &\mapsto \langle 0, 0, 1 \rangle \\ S_5 &\mapsto \langle 1, 0, 1 \rangle \end{aligned}$$

2. A **one-hot encoding** represents the i -th of n states as a sequence X st. $X_i = 1$ and $X_j = 0$ for $j \neq i$, e.g.,

$$\begin{aligned} S_0 &\mapsto \langle 1, 0, 0, 0, 0, 0 \rangle \\ S_1 &\mapsto \langle 0, 1, 0, 0, 0, 0 \rangle \\ S_2 &\mapsto \langle 0, 0, 1, 0, 0, 0 \rangle \\ S_3 &\mapsto \langle 0, 0, 0, 1, 0, 0 \rangle \\ S_4 &\mapsto \langle 0, 0, 0, 0, 1, 0 \rangle \\ S_5 &\mapsto \langle 0, 0, 0, 0, 0, 1 \rangle \end{aligned}$$

noting that we have a larger state (i.e., n bits instead of $\lceil \log_2(n) \rceil$), *but*

- ▶ transition between states is easier, *and*
- ▶ switching behaviour (and hence power consumption) is reduced.

Notes:

Examples (1)

A modulo 6 ascending counter

Question

Design an FSM that acts as a cyclic counter modulo n (rather than 2^n as before). If $n = 6$ for example, we want a component whose output r steps through values

$$0, 1, 2, 3, 4, 5, 0, 1, \dots,$$

with the modular reduction representing control behaviour (versus the uncontrolled counter that was cyclic by default).

Notes:

Algorithm (tabular)			Algorithm (diagram)		
	δ	ω	<pre> graph TD start((start)) --> S0((S0)) S0 -- ε --> S1((S1)) S1 -- ε --> S2((S2)) S2 -- ε --> S3((S3)) S3 -- ε --> S4((S4)) S4 -- ε --> S5((S5)) S5 -- ε --> S0 </pre>		
Q	Q'	r			
S_0	S_1	0			
S_1	S_2	1			
S_2	S_3	2			
S_3	S_4	3			
S_4	S_5	4			
S_5	S_0	5			

Notes:

- To implement the design via the framework, we need a state assignment step:

- There are 6 abstract labels

$$\begin{array}{ll} S_0 & \mapsto 0 \\ S_1 & \mapsto 1 \\ S_2 & \mapsto 2 \\ S_3 & \mapsto 3 \\ S_4 & \mapsto 4 \\ S_5 & \mapsto 5 \end{array}$$

representing the integers $0, 1, \dots, 5$.

- Since $2^3 = 8 > 6$, we can represent them using 6 concrete values, namely

$$\begin{array}{llll} S_0 & \mapsto & \langle 0, 0, 0 \rangle & \equiv 000_{(2)} \\ S_1 & \mapsto & \langle 1, 0, 0 \rangle & \equiv 001_{(2)} \\ S_2 & \mapsto & \langle 0, 1, 0 \rangle & \equiv 010_{(2)} \\ S_3 & \mapsto & \langle 1, 1, 0 \rangle & \equiv 011_{(2)} \\ S_4 & \mapsto & \langle 0, 0, 1 \rangle & \equiv 100_{(2)} \\ S_5 & \mapsto & \langle 1, 0, 1 \rangle & \equiv 101_{(2)} \end{array}$$

and capture

1. $Q = \langle Q_0, Q_1, Q_2 \rangle \equiv$ the current state
2. $Q' = \langle Q'_0, Q'_1, Q'_2 \rangle \equiv$ the next state

in a 3-bit register (i.e., via 3 latches or flip-flops).

Notes:

Algorithm (truth table)

Rewriting the abstract labels yields the following concrete truth table


			δ			ω		
Q_2	Q_1	Q_0	Q'_2	Q'_1	Q'_0	r_2	r_1	r_0
0	0	0	0	0	1	0	0	0
0	0	1	0	1	0	0	0	1
0	1	0	0	1	1	0	1	0
0	1	1	1	0	0	0	1	1
1	0	0	1	0	1	1	0	0
1	0	1	0	0	0	1	0	1
1	1	0	?	?	?	?	?	?
1	1	1	?	?	?	?	?	?

noting that our state assignment means $r = Q$, st. $r = \omega(Q) = Q$ is basically just the identity function (so we'll ignore it).

Notes:

Circuit (δ)

 Translating the truth table into a set of Karnaugh maps



yields the following Boolean expressions for δ :

$$\begin{aligned} Q'_2 &= (\quad \quad \quad Q_1 \quad \wedge \quad \quad Q_0 \quad) \vee \\ &\quad (\quad Q_2 \quad \wedge \quad \quad \neg Q_0 \quad) \\ Q'_1 &= (\neg Q_2 \quad \wedge \quad \neg Q_1 \quad \wedge \quad Q_0 \quad) \vee \\ &\quad (\quad \quad Q_1 \quad \wedge \quad \neg Q_0 \quad) \\ Q'_0 &= (\quad \quad \quad \neg Q_0 \quad) \end{aligned}$$

Notes:

Question

Design an FSM that controls traffic lights at the intersection of two roads (a main road and an access road); it should


- stop cars crashing into each other, so the behaviour should see
 - ▶ green on main road and red on access road, then
 - ▶ amber on main road and red on access road, then
 - ▶ red on main road and amber on access road, then
 - ▶ red on main road and green on access road, then
 - ▶ red on main road and amber on access road, then
 - ▶ amber on main road and red on access road,and then cycle, and
- allow an emergency stop button to force red on both main and access roads while pushed, then reset the system into an initial start state when released.

Notes:

Algorithm (tabular)

Q	δ		ω					
	Q'		M_g	M_a	M_r	A_g	A_a	A_r
	$rst = 0$	$rst = 1$						
S_0	S_1	S_6	1	0	0	0	0	1
S_1	S_2	S_6	0	1	0	0	0	1
S_2	S_3	S_6	0	0	1	0	1	0
S_3	S_4	S_6	0	0	1	1	0	0
S_4	S_5	S_6	0	0	1	0	1	0
S_5	S_0	S_6	0	1	0	0	0	1
S_6	S_0	S_6	0	0	1	0	0	1

Algorithm (diagram)

 

Notes:

Algorithm (truth table)


Rewriting the abstract labels yields the following concrete truth table:

	δ			ω								
rst	Q_2	Q_1	Q_0	Q'_2	Q'_1	Q'_0	M_g	M_a	M_r	A_g	A_a	A_r
0	0	0	0	0	0	1	1	0	0	0	0	1
0	0	0	1	0	1	0	0	1	0	0	0	1
0	0	1	0	0	1	1	0	0	1	0	1	0
0	0	1	1	1	0	0	0	0	1	1	0	0
0	1	0	0	1	0	1	0	0	1	0	1	0
0	1	0	1	0	0	0	0	1	0	0	0	1
0	1	1	0	0	0	0	0	0	1	0	0	1
0	1	1	1	?	?	?	?	?	?	?	?	?
1	0	0	0	1	1	0	1	0	0	0	0	1
1	0	0	1	1	1	0	0	1	0	0	0	1
1	0	1	0	1	1	0	0	0	1	0	1	0
1	0	1	1	1	1	0	0	0	1	1	0	0
1	1	0	0	1	1	0	0	0	1	0	1	0
1	1	0	1	1	1	0	0	0	1	0	0	1
1	1	1	0	1	1	0	0	0	1	0	1	0
1	1	1	1	1	1	0	0	1	0	0	0	1
1	1	1	0	1	1	0	0	0	1	0	0	1
1	1	1	1	?	?	?	?	?	?	?	?	?

Notes:

Circuit (δ)

 Translating the truth table into a set of Karnaugh maps




yields the following Boolean expressions for δ :

$$\begin{aligned}
 Q'_2 &= (rst \wedge Q_2 \wedge \neg Q_1 \wedge \neg Q_0) \vee \\
 &\quad (rst \wedge Q_2 \wedge Q_1 \wedge Q_0) \\
 Q'_1 &= (rst \wedge \neg Q_2 \wedge \neg Q_1 \wedge Q_0) \vee \\
 &\quad (rst \wedge \neg Q_2 \wedge Q_1 \wedge \neg Q_0) \\
 Q'_0 &= (\neg rst \wedge \neg Q_2 \wedge \neg Q_1 \wedge \neg Q_0) \vee \\
 &\quad (\neg rst \wedge \neg Q_2 \wedge Q_1 \wedge \neg Q_0)
 \end{aligned}$$

Notes:

Circuit (ω)

 Translating the truth table into a set of Karnaugh maps



yields the following Boolean expressions for ω :

$$\begin{aligned}
 M_g &= (\neg Q_2 \wedge \neg Q_1 \wedge \neg Q_0) & A_g &= (Q_1 \wedge Q_0) \\
 M_a &= (\neg Q_1 \wedge Q_0) & A_a &= (\neg Q_2 \wedge Q_1 \wedge \neg Q_0) \vee (Q_2 \wedge \neg Q_1 \wedge \neg Q_0) \\
 M_r &= (Q_1 \wedge \neg Q_0) \vee (Q_2 \wedge \neg Q_0) & A_r &= (\neg Q_2 \wedge \neg Q_1 \wedge Q_0) \vee (\neg Q_1 \wedge Q_0) \vee (Q_2 \wedge Q_1)
 \end{aligned}$$

Notes:

Conclusions

► Take away points:

1. We've linked together theory and practice: FSMs are abstract computational models, but we've used them to solve concrete problems.
2. We've *only* used concepts in digital logic that we know how to construct right from the transistor-level; there is no "magic" going on behind the scenes.
3. Clearly the examples are limited, but a fundamentally similar framework can be used for more complex computational machines.

Notes:

Additional Reading

- ▶ *Wikipedia: Finite State Machine (FSM)*. . URL: http://en.wikipedia.org/wiki/Finite-state_machine.
- ▶ D. Page. “Chapter 2: Basics of digital logic”. In: *A Practical Introduction to Computer Architecture*. 1st ed. Springer-Verlag, 2009.
- ▶ M. Sipster. “Chapter 1: Regular languages”. In: *Introduction to the Theory of Computation*. 2nd ed. Thomson Course Technology, 2006.

Notes:

References

- [1] *Wikipedia: Finite State Machine (FSM)*. URL: http://en.wikipedia.org/wiki/Finite-state_machine (see p. 45).
- [2] D. Page. “Chapter 2: Basics of digital logic”. In: *A Practical Introduction to Computer Architecture*. 1st ed. Springer-Verlag, 2009 (see p. 45).
- [3] M. Sipster. “Chapter 1: Regular languages”. In: *Introduction to the Theory of Computation*. 2nd ed. Thomson Course Technology, 2006 (see p. 45).

Notes: