

Intro. to Computer Architecture

Daniel Page

Department of Computer Science,
University Of Bristol,
Merchant Venturers Building,
Woodland Road,
Bristol, BS8 1UB. UK.
(csdsp@bristol.ac.uk)

January 9, 2018

Keep in mind there are *two* PDFs available (of which this is the latter):

1. a PDF of examinable material used as lecture slides, and
2. a PDF of non-examinable, extra material:
 - ▶ the associated notes page may be pre-populated with extra, written explanation of material covered in lecture(s), plus
 - ▶ anything with a “grey’ed out” header/footer represents extra material which is useful and/or interesting but out of scope (and hence not covered).

Notes:

Notes:

► **Agenda:**

1. comments, questions, recap, then
2. some special-purpose implementation techniques and related trade-offs, namely
 - improving the functionality of a ripple-carry adder, and
 - reducing the latency of a ripple-carry adder (via **carry look-ahead** addition).

Notes:

► **Recap:** we produced the following algorithm for (ripple-carry) addition

Algorithm

Input: Two unsigned, n -digit, base- b integers x and y , and a 1-digit carry-in $c_i \in \{0, 1\}$


Output: An unsigned, n -digit, base- b integer $r = x + y$, and a 1-digit carry-out $c_o \in \{0, 1\}$

```

1  $r \leftarrow 0, c_0 \leftarrow c_i$ 
2 for  $i = 0$  upto  $n - 1$  step  $+1$  do
3    $r_i \leftarrow (x_i + y_i + c_i) \bmod b$ 
4   if  $(x_i + y_i + c_i) < b$  then  $c_{i+1} \leftarrow 0$  else  $c_{i+1} \leftarrow 1$ 
5 end
6  $c_o \leftarrow c_n$ 
7 return  $r, c_o$ 
```

Notes:

 - **Recap:** we produced the following design for (ripple-carry) addition



based on existence of a full-adder cell.

Notes:

Boolean algebra + computer arithmetic \leadsto design trade-offs (1)
Area vs. functionality

- **Question:** how can we support subtraction?

Notes:

- **Question:** how can we support subtraction?
- **Solution:** the algorithm is basically the same

Algorithm

Input: Two unsigned, n -digit, base- b integers x and y , and a 1-digit borrow-in $bi \in \{0, 1\}$
Output: An unsigned, n -digit, base- b integer $r = x - y$, and a 1-digit borrow-out $bo \in \{0, 1\}$

```


1  $r \leftarrow 0, c_0 \leftarrow bi$ 
2 for  $i = 0$  upto  $n - 1$  step  $+1$  do
3    $r_i \leftarrow (x_i - y_i - c_i) \bmod b$ 
4   if  $(x_i - y_i - c_i) \geq 0$  then  $c_{i+1} \leftarrow 0$  else  $c_{i+1} \leftarrow 1$ 
5 end
6  $bo \leftarrow c_n$ 
7 return  $r, bo$ 

```

Notes:

- **Question:** how can we support subtraction?
- **Solution:** the design is basically the same we produced the following design


Circuit

 

albeit now based on existence of an alternative, full-subtractor cell.

Notes:

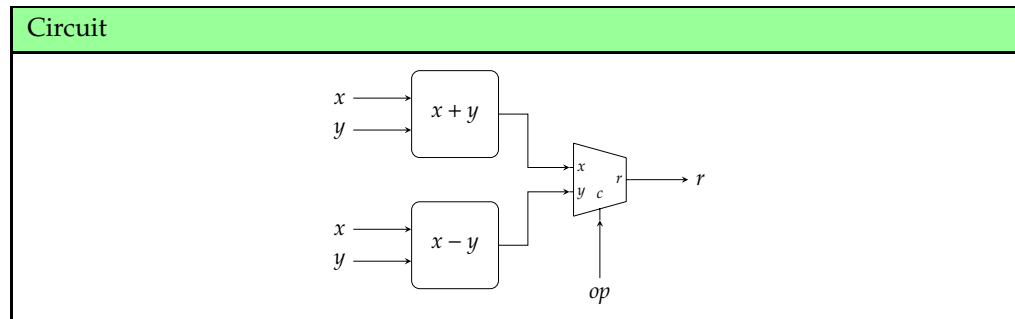- **Question:** how can we support subtraction *and* addition?
- **Solution #1:** compute *both*, then select which we want, i.e.,




st.

$$r = \begin{cases} x + y & \text{if } op = 0 \\ x - y & \text{if } op = 1 \end{cases} ,$$

ignoring the carry/borrow in and out for the moment.

Notes:

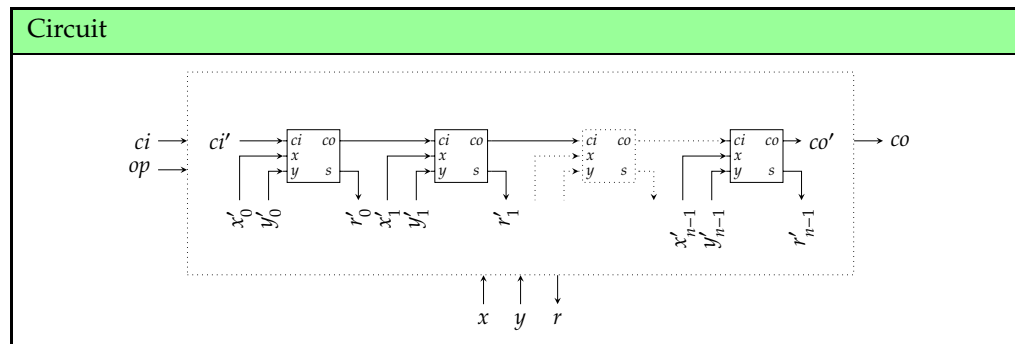- **Question:** how can we support subtraction *and* addition?
- **Solution #2:** we know $x - y \equiv x + (-y)$ and can *already* compute $x + y$, so



given we want

$$r = \begin{cases} x + y + ci & \text{if } op = 0 \\ x - y - ci & \text{if } op = 1 \end{cases} ,$$

we just need to consider how x' , y' and ci' are controlled?

Notes:

Definition

The term two's-complement can be used as a noun (i.e., to describe the *representation*) or a verb (i.e., to describe an *operation*): the latter case defines “taking the two's-complement of x ” to mean negating x and thus computing the representation of $-x$. To do so, we compute $-x \mapsto \neg x + 1$.

► So,

op	ci	r			
0	0	x	+	y	+ ci
0	1	x	+	y	+ ci
1	0	x	−	y	− ci
1	1	x	−	y	− ci

Notes:

Definition

The term two's-complement can be used as a noun (i.e., to describe the *representation*) or a verb (i.e., to describe an *operation*): the latter case defines “taking the two's-complement of x ” to mean negating x and thus computing the representation of $-x$. To do so, we compute $-x \mapsto \neg x + 1$.

► So,

op	ci	r			
0	0	x	+	y	+ 0
0	1	x	+	y	+ 1
1	0	x	−	y	− 0
1	1	x	−	y	− 1

Notes:

Definition

The term two's-complement can be used as a noun (i.e., to describe the *representation*) or a verb (i.e., to describe an *operation*): the latter case defines “taking the two's-complement of x ” to mean negating x and thus computing the representation of $-x$. To do so, we compute $-x \mapsto \neg x + 1$.

► So,

op	ci	r			
0	0	x	+	y	+ 0
0	1	x	+	y	+ 1
1	0	x	+	$\neg y + 1$	- 0
1	1	x	+	$\neg y + 1$	- 1

Notes:

Definition

The term two's-complement can be used as a noun (i.e., to describe the *representation*) or a verb (i.e., to describe an *operation*): the latter case defines “taking the two's-complement of x ” to mean negating x and thus computing the representation of $-x$. To do so, we compute $-x \mapsto \neg x + 1$.

► So,

op	ci	r			
0	0	x	+	y	+ 0
0	1	x	+	y	+ 1
1	0	x	+	$\neg y$	+ 1
1	1	x	+	$\neg y$	+ 0

Notes:

Definition

The term two's-complement can be used as a noun (i.e., to describe the *representation*) or a verb (i.e., to describe an *operation*): the latter case defines "taking the two's-complement of x " to mean negating x and thus computing the representation of $-x$. To do so, we compute $-x \mapsto \neg x + 1$.

► So,

op	ci	r			
0	0	x	+	y	+ 0
0	1	x	+	y	+ 1
1	0	x	+	$\neg y$	+ 1
1	1	x	+	$\neg y$	+ 0

and then just translate via

op	ci	x_i	y_i	ci'	x'_i	y'_i
0	0	0	0	0	0	0
0	1	1	1	1	1	1
1	0	0	0	1	0	1
1	1	1	1	0	1	0


i.e., $ci' = ci \oplus op$, $x'_i = x_i$, and $y'_i = y_i \oplus op$...

Notes:

Boolean algebra + computer arithmetic \leadsto design trade-offs (4) Area vs. functionality

► ... to yield

Circuit

 


Notes:

- The comparison with a single ripple-carry adder is easy to see: the combined design includes $n + 1$ additional XORs, the area related to which is traded-off against support for subtraction. In contrast, the comparison with the separate design (i.e., a ripple-carry adder plus a subtractor) is a more subtle wrt. the functionality metric. The point is that although both support subtraction, the former is clearly unable to simultaneously perform addition and subtraction, whereas the latter *might* be.

Boolean algebra + computer arithmetic \leadsto design trade-offs (4)

Area vs. functionality

► ... to yield

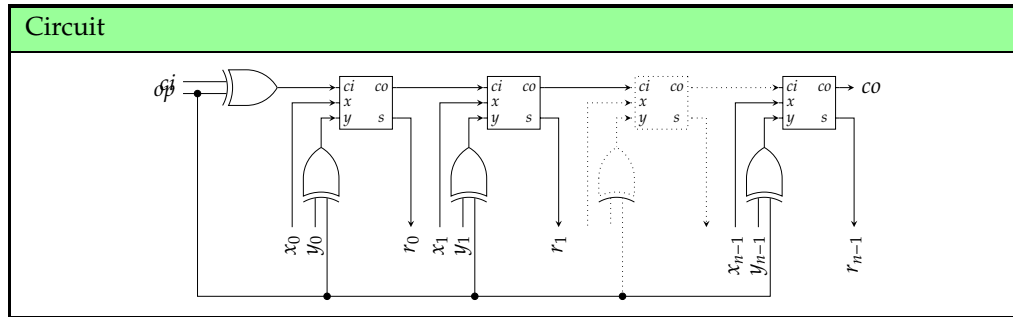

► Question(s):

1. what are the design trade-offs here, and/or
2. how do we evaluate this design vs. alternatives?

► Answer(s):

- ve: : higher area vs. ripple-carry adder
- +ve: : greater functionality vs. ripple-carry adder


Notes:

- The comparison with a single ripple-carry adder is easy to see: the combined design includes $n + 1$ additional XORs, the area related to which is traded-off against support for subtraction. In contrast, the comparison with the separate design (i.e., a ripple-carry adder plus a subtractor) is a more subtle wrt. the functionality metric. The point is that although both support subtraction, the former is clearly unable to simultaneously perform addition and subtraction, whereas the latter *might* be.

Boolean algebra + computer arithmetic \leadsto design trade-offs (4)

Area vs. functionality

► ... to yield

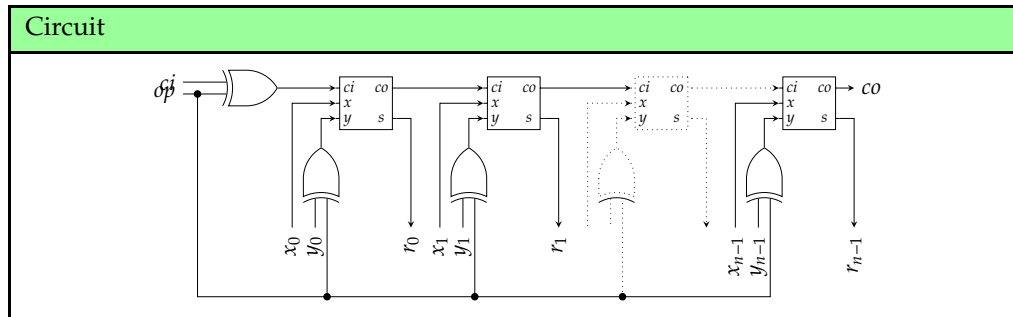

► Question(s):

1. what are the design trade-offs here, and/or
2. how do we evaluate this design vs. alternatives?

► Answer(s):

- +ve: : lower area vs. ripple-carry adder plus subtractor
- ve: : lesser functionality vs. ripple-carry adder plus subtractor

Notes:

- The comparison with a single ripple-carry adder is easy to see: the combined design includes $n + 1$ additional XORs, the area related to which is traded-off against support for subtraction. In contrast, the comparison with the separate design (i.e., a ripple-carry adder plus a subtractor) is a more subtle wrt. the functionality metric. The point is that although both support subtraction, the former is clearly unable to simultaneously perform addition and subtraction, whereas the latter *might* be.

Definition

latency, *n.* the interval between the reception of a stimulus and the response to that stimulus.

– OED (<http://www.oed.com>)

Notes:

Definition

latency, *n.* the interval between the reception of a stimulus and the response to that stimulus.

– OED (<http://www.oed.com>)

- **Question:** what is the latency of ripple-carry addition?

Notes:

Definition

latency, *n.* the interval between the reception of a stimulus and the response to that stimulus.

– OED (<http://www.oed.com>)

- ▶ **Question:** what is the latency of ripple-carry addition?
- ▶ **Solution:** $O(n)$.

Notes:

Definition

latency, *n.* the interval between the reception of a stimulus and the response to that stimulus.

– OED (<http://www.oed.com>)

- ▶ **Question:** what is the latency of ripple-carry addition?
- ▶ **Solution:** $O(n)$.
- ▶ **Question:** can we *improve* this somehow?

Notes:

Definition

latency, *n.* the interval between the reception of a stimulus and the response to that stimulus.

– OED (<http://www.oed.com>)

- ▶ **Question:** what is the latency of ripple-carry addition?
- ▶ **Solution:** $O(n)$.
- ▶ **Question:** can we *improve* this somehow?
- ▶ **Solution:** yes ...

Notes:

Boolean algebra + computer arithmetic \leadsto design trade-offs (6)

- ▶ **Observation:** the carry-chain between cells *dictates* latency.
- ▶ **Idea:** *decouple* computation of the carry from the sum.
 - ▶ We know *something* about how the i -th cell behaves in isolation, i.e.,
 1. $x_i + y_i > b - 1 \Rightarrow$ it *generates* a carry
 2. $x_i + y_i = b - 1 \Rightarrow$ it *propagates* a carry
 3. $x_i + y_i < b - 1 \Rightarrow$ it *absorbs* a carry
 - ▶ For $b = 2$, imagine g_i and p_i tell us whether the stage generate or propagate a carry; then

$$\begin{aligned} g_i &= x_i \wedge y_i \\ p_i &= x_i \oplus y_i \end{aligned}$$

and we have that

$$c_{i+1} = g_i \vee (c_i \wedge p_i)$$

where, again, $c_0 = ci$ and we produce a carry-out $c_n = co$.


Notes:

Example

Unwinding the recursion, the carry into each cell is described by

$$\begin{aligned} c_0 &= ci \\ c_1 &= g_0 \vee (ci \wedge p_0) \\ c_2 &= g_1 \vee (g_0 \wedge p_1) \vee (ci \wedge p_0 \wedge p_1) \\ c_3 &= g_2 \vee (g_1 \wedge p_2) \vee (g_0 \wedge p_1 \wedge p_2) \vee (ci \wedge p_0 \wedge p_1 \wedge p_2) \\ &\vdots \end{aligned}$$

 which *looks* horrendous, but notice that the general structure is something like




Notes:

Boolean algebra + computer arithmetic \leadsto design trade-offs (8) Area vs. latency


► **Solution:** a **carry look-ahead** adder design

Circuit

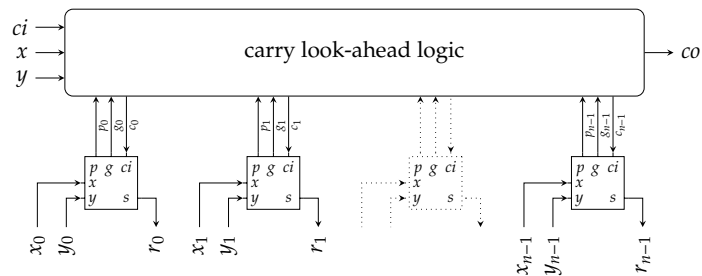

Notes:

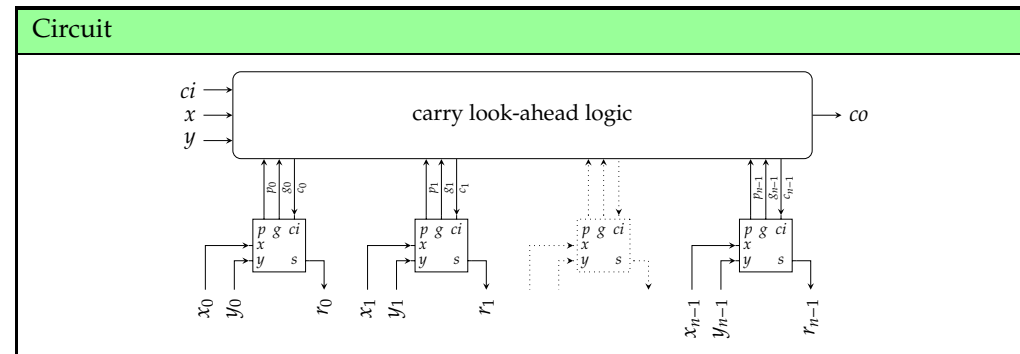- **Solution:** a **carry look-ahead** adder design



- **Question(s):**

1. what are the design trade-offs here, and/or
2. how do we evaluate this design vs. alternatives?

- **Answer(s):**

- ve: : higher area vs. ripple-carry adder
- +ve: : lower latency vs. ripple-carry adder

Conclusions

- **Take away points:**

1. We've seen two concrete design trade-offs, namely

higher area \leadsto greater functionality

higher area \leadsto lower latency

noting that each design was still *correct*.

2. To produce the associated designs, we've had to understand

- the problem domain (e.g., computer arithmetic),
- the problem specification (e.g., design constraints, such as a preference for low latency),
- the resources and techniques available (e.g., Boolean operators)
- ...

which is subtle, but critical: the best results are produced by application of richer understanding (of this unit, CS in general, and beyond).

Notes:

Notes:

Additional Reading

- ▶ [Wikipedia: Computer Arithmetic](http://en.wikipedia.org/wiki/Category:Computer_arithmetic). URL: http://en.wikipedia.org/wiki/Category:Computer_arithmetic.
- ▶ D. Page. “Chapter 7: Arithmetic and logic”. In: *A Practical Introduction to Computer Architecture*. 1st ed. Springer-Verlag, 2009.
- ▶ B. Parhami. “Part 2: Addition/subtraction”. In: *Computer Arithmetic: Algorithms and Hardware Designs*. 1st ed. Oxford University Press, 2000.

Notes:

References

- [1] [Wikipedia: Computer Arithmetic](http://en.wikipedia.org/wiki/Category:Computer_arithmetic). URL: http://en.wikipedia.org/wiki/Category:Computer_arithmetic (see p. 57).
- [2] D. Page. “Chapter 7: Arithmetic and logic”. In: *A Practical Introduction to Computer Architecture*. 1st ed. Springer-Verlag, 2009 (see p. 57).
- [3] B. Parhami. “Part 2: Addition/subtraction”. In: *Computer Arithmetic: Algorithms and Hardware Designs*. 1st ed. Oxford University Press, 2000 (see p. 57).

Notes: