

# Intro. to Computer Architecture

Daniel Page

Department of Computer Science,  
University Of Bristol,  
Merchant Venturers Building,  
Woodland Road,  
Bristol, BS8 1UB. UK.  
([csdsp@bristol.ac.uk](mailto:csdsp@bristol.ac.uk))

January 9, 2018

Keep in mind there are *two* PDFs available (of which this is the latter):

1. a PDF of examinable material used as lecture slides, and
2. a PDF of non-examinable, extra material:
  - ▶ the associated notes page may be pre-populated with extra, written explanation of material covered in lecture(s), plus
  - ▶ anything with a “grey’ed out” header/footer represents extra material which is useful and/or interesting but out of scope (and hence not covered).

Notes:

Notes:

- **Recap:** our goal is to implement a bit-serial multiplier, i.e.,

Algorithm	Circuit
<p><b>Input:</b> Two unsigned, <math>n</math>-bit, base-2 integers <math>x</math> and <math>y</math>  <b>Output:</b> An unsigned, <math>2n</math>-bit, base-2 integer <math>r = y \cdot x</math></p> <pre> 1 <math>r \leftarrow 0</math> 2 <b>for</b> <math>i = n - 1</math> <b>downto</b> 0 <b>step</b> -1 <b>do</b> 3   <math>r \leftarrow 2 \cdot r</math> 4   <b>if</b> <math>y_i = 1</math> <b>then</b> 5     <math>r \leftarrow r + x</math> 6   <b>end</b> 7 <b>end</b> 8 <b>return</b> <math>r</math> </pre>	

as a case-study of data- and control-paths; we more or less have the data-path, but what about the control-path ...

Notes:

Question
<p>Design an FSM-based component that replicates the behaviour of a loop counter, for example <math>i</math> within a C-style <b>for</b> loop such as</p> <pre> 1 <b>for</b>( <b>int</b> <math>i = m</math>; <math>i &lt; n</math>; <math>i++</math> ) { 2   ... 3 } </pre> <p>noting that</p> <ol style="list-style-type: none"> <li>1. we'll look at <i>a</i> solution, not <i>all</i> solutions,</li> <li>2. we'll need a mechanism that informs us when this is, plus also allows us to start iteration,</li> <li>3. we'll allow the loop counter <math>i</math> to equal <math>n</math> once the loop is complete (as is the case in C), and</li> <li>4. we'll consider 4-bit values of <math>i</math>, <math>m</math> and <math>n</math> st. this design is basically an "upgrade" to the previous, uncontrolled counter and the <math>n</math> (the loop bound) here <b>isn't</b> necessarily <math>n</math> (the size of <math>x</math> and <math>y</math>) from the multiplier algorithm!</li> </ol>

Notes:

## A loop counter (1)

A control protocol

- ▶ **Question:** given a user  $C_1$  of some component  $C_2$ , how does
  1.  $C_2$  know when to start computation (e.g., when any input  $x$  is available), and
  2.  $C_1$  know when computation has finished (e.g., when any output  $r = f(x)$  is available).
- ▶ **Solution(s):**
  1. use a shared clock signal to synchronise events somehow, or
  2. use a simple **control protocol** based on two signals
    - 2.1 *req* (or **request**), and
    - 2.2 *ack* (or **acknowledge**).


Notes:

- A shared clock might *seem* the ideal option, but there are (at least) two scenarios where it doesn't work out so well:
  1. when  $C_2$  and  $C_1$  are physically separate, since synchronised clock distribution is hard(er), and
  2. when the number of steps  $C_2$  takes is variable, since even if  $C_2$  and  $C_1$  are synchronised the latter still cannot tell when the former has completed a given computation.

## A loop counter (2)

A control protocol

### Algorithm

 


Notes:

- - Initially, *req* = 0 and *ack* = 0.
  - When  $C_1$  wants to compute something, it first drives any input values (say  $x$ ) then sets *req* = 1 to signal they are ready for use.
  - $C_2$  notices this, and starts computation. Eventually the computation is complete, meaning  $r = f(x)$ ; to signal this to  $C_1$ , it sets *ack* = 1.
  - $C_1$  notices this, and concludes that the computation is finished: it latches  $r$ , and finally sets *req* = 0.
  - $C_2$  notices this, and concludes that the computation is finished: it sets *ack* = 0 then waits for the next request.
  - $C_1$  notices this, and proceeds to use  $r$  for whatever purpose it was computed.
  - Since both *req* = 0 and *ack* = 0, the process can now begin again from the start whenever  $C_1$  needs to perform another computation.

## A loop counter (2)

A control protocol

### Algorithm

 


#### Notes:

- Initially,  $req = 0$  and  $ack = 0$ .
- When  $C_1$  wants to compute something, it first drives any input values (say  $x$ ) then sets  $req = 1$  to signal they are ready for use.
- $C_2$  notices this, and starts computation. Eventually the computation is complete, meaning  $r = f(x)$ ; to signal this to  $C_1$ , it sets  $ack = 1$ .
- $C_1$  notices this, and concludes that the computation is finished: it latches  $r$ , and finally sets  $req = 0$ .
- $C_2$  notices this, and concludes that the computation is finished: it sets  $ack = 0$  then waits for the next request.
- $C_1$  notices this, and proceeds to use  $r$  for whatever purpose it was computed.
- Since both  $req = 0$  and  $ack = 0$ , the process can now begin again from the start whenever  $C_1$  needs to perform another computation.

## A loop counter (2)

A control protocol

### Algorithm

 


#### Notes:

- Initially,  $req = 0$  and  $ack = 0$ .
- When  $C_1$  wants to compute something, it first drives any input values (say  $x$ ) then sets  $req = 1$  to signal they are ready for use.
- $C_2$  notices this, and starts computation. Eventually the computation is complete, meaning  $r = f(x)$ ; to signal this to  $C_1$ , it sets  $ack = 1$ .
- $C_1$  notices this, and concludes that the computation is finished: it latches  $r$ , and finally sets  $req = 0$ .
- $C_2$  notices this, and concludes that the computation is finished: it sets  $ack = 0$  then waits for the next request.
- $C_1$  notices this, and proceeds to use  $r$  for whatever purpose it was computed.
- Since both  $req = 0$  and  $ack = 0$ , the process can now begin again from the start whenever  $C_1$  needs to perform another computation.

## A loop counter (2)

A control protocol

### Algorithm

 


#### Notes:

- Initially,  $req = 0$  and  $ack = 0$ .
- When  $C_1$  wants to compute something, it first drives any input values (say  $x$ ) then sets  $req = 1$  to signal they are ready for use.
- $C_2$  notices this, and starts computation. Eventually the computation is complete, meaning  $r = f(x)$ ; to signal this to  $C_1$ , it sets  $ack = 1$ .
- $C_1$  notices this, and concludes that the computation is finished: it latches  $r$ , and finally sets  $req = 0$ .
- $C_2$  notices this, and concludes that the computation is finished: it sets  $ack = 0$  then waits for the next request.
- $C_1$  notices this, and proceeds to use  $r$  for whatever purpose it was computed.
- Since both  $req = 0$  and  $ack = 0$ , the process can now begin again from the start whenever  $C_1$  needs to perform another computation.

## A loop counter (2)

A control protocol

### Algorithm

 


#### Notes:

- Initially,  $req = 0$  and  $ack = 0$ .
- When  $C_1$  wants to compute something, it first drives any input values (say  $x$ ) then sets  $req = 1$  to signal they are ready for use.
- $C_2$  notices this, and starts computation. Eventually the computation is complete, meaning  $r = f(x)$ ; to signal this to  $C_1$ , it sets  $ack = 1$ .
- $C_1$  notices this, and concludes that the computation is finished: it latches  $r$ , and finally sets  $req = 0$ .
- $C_2$  notices this, and concludes that the computation is finished: it sets  $ack = 0$  then waits for the next request.
- $C_1$  notices this, and proceeds to use  $r$  for whatever purpose it was computed.
- Since both  $req = 0$  and  $ack = 0$ , the process can now begin again from the start whenever  $C_1$  needs to perform another computation.

## A loop counter (2)

A control protocol

### Algorithm

 


#### Notes:

- Initially,  $req = 0$  and  $ack = 0$ .
- When  $C_1$  wants to compute something, it first drives any input values (say  $x$ ) then sets  $req = 1$  to signal they are ready for use.
- $C_2$  notices this, and starts computation. Eventually the computation is complete, meaning  $r = f(x)$ ; to signal this to  $C_1$ , it sets  $ack = 1$ .
- $C_1$  notices this, and concludes that the computation is finished: it latches  $r$ , and finally sets  $req = 0$ .
- $C_2$  notices this, and concludes that the computation is finished: it sets  $ack = 0$  then waits for the next request.
- $C_1$  notices this, and proceeds to use  $r$  for whatever purpose it was computed.
- Since both  $req = 0$  and  $ack = 0$ , the process can now begin again from the start whenever  $C_1$  needs to perform another computation.

## A loop counter (2)

A control protocol

### Algorithm

 


#### Notes:

- Initially,  $req = 0$  and  $ack = 0$ .
- When  $C_1$  wants to compute something, it first drives any input values (say  $x$ ) then sets  $req = 1$  to signal they are ready for use.
- $C_2$  notices this, and starts computation. Eventually the computation is complete, meaning  $r = f(x)$ ; to signal this to  $C_1$ , it sets  $ack = 1$ .
- $C_1$  notices this, and concludes that the computation is finished: it latches  $r$ , and finally sets  $req = 0$ .
- $C_2$  notices this, and concludes that the computation is finished: it sets  $ack = 0$  then waits for the next request.
- $C_1$  notices this, and proceeds to use  $r$  for whatever purpose it was computed.
- Since both  $req = 0$  and  $ack = 0$ , the process can now begin again from the start whenever  $C_1$  needs to perform another computation.

## A loop counter (2)

A control protocol

### Algorithm

 


#### Notes:

- Initially,  $req = 0$  and  $ack = 0$ .
- When  $C_1$  wants to compute something, it first drives any input values (say  $x$ ) then sets  $req = 1$  to signal they are ready for use.
- $C_2$  notices this, and starts computation. Eventually the computation is complete, meaning  $r = f(x)$ ; to signal this to  $C_1$ , it sets  $ack = 1$ .
- $C_1$  notices this, and concludes that the computation is finished: it latches  $r$ , and finally sets  $req = 0$ .
- $C_2$  notices this, and concludes that the computation is finished: it sets  $ack = 0$  then waits for the next request.
- $C_1$  notices this, and proceeds to use  $r$  for whatever purpose it was computed.
- Since both  $req = 0$  and  $ack = 0$ , the process can now begin again from the start whenever  $C_1$  needs to perform another computation.

## A loop counter (2)

A control protocol

### Algorithm

 


#### Notes:

- Initially,  $req = 0$  and  $ack = 0$ .
- When  $C_1$  wants to compute something, it first drives any input values (say  $x$ ) then sets  $req = 1$  to signal they are ready for use.
- $C_2$  notices this, and starts computation. Eventually the computation is complete, meaning  $r = f(x)$ ; to signal this to  $C_1$ , it sets  $ack = 1$ .
- $C_1$  notices this, and concludes that the computation is finished: it latches  $r$ , and finally sets  $req = 0$ .
- $C_2$  notices this, and concludes that the computation is finished: it sets  $ack = 0$  then waits for the next request.
- $C_1$  notices this, and proceeds to use  $r$  for whatever purpose it was computed.
- Since both  $req = 0$  and  $ack = 0$ , the process can now begin again from the start whenever  $C_1$  needs to perform another computation.

## A loop counter (2)

A control protocol

### Algorithm

 


#### Notes:

- Initially,  $req = 0$  and  $ack = 0$ .
- When  $C_1$  wants to compute something, it first drives any input values (say  $x$ ) then sets  $req = 1$  to signal they are ready for use.
- $C_2$  notices this, and starts computation. Eventually the computation is complete, meaning  $r = f(x)$ ; to signal this to  $C_1$ , it sets  $ack = 1$ .
- $C_1$  notices this, and concludes that the computation is finished: it latches  $r$ , and finally sets  $req = 0$ .
- $C_2$  notices this, and concludes that the computation is finished: it sets  $ack = 0$  then waits for the next request.
- $C_1$  notices this, and proceeds to use  $r$  for whatever purpose it was computed.
- Since both  $req = 0$  and  $ack = 0$ , the process can now begin again from the start whenever  $C_1$  needs to perform another computation.

## A loop counter (2)

A control protocol

### Algorithm

 

#### Notes:


- Initially,  $req = 0$  and  $ack = 0$ .
- When  $C_1$  wants to compute something, it first drives any input values (say  $x$ ) then sets  $req = 1$  to signal they are ready for use.
- $C_2$  notices this, and starts computation. Eventually the computation is complete, meaning  $r = f(x)$ ; to signal this to  $C_1$ , it sets  $ack = 1$ .
- $C_1$  notices this, and concludes that the computation is finished: it latches  $r$ , and finally sets  $req = 0$ .
- $C_2$  notices this, and concludes that the computation is finished: it sets  $ack = 0$  then waits for the next request.
- $C_1$  notices this, and proceeds to use  $r$  for whatever purpose it was computed.
- Since both  $req = 0$  and  $ack = 0$ , the process can now begin again from the start whenever  $C_1$  needs to perform another computation.



## A loop counter (2)

A control protocol

### Algorithm

 


#### Notes:

- Initially,  $req = 0$  and  $ack = 0$ .
- When  $C_1$  wants to compute something, it first drives any input values (say  $x$ ) then sets  $req = 1$  to signal they are ready for use.
- $C_2$  notices this, and starts computation. Eventually the computation is complete, meaning  $r = f(x)$ ; to signal this to  $C_1$ , it sets  $ack = 1$ .
- $C_1$  notices this, and concludes that the computation is finished: it latches  $r$ , and finally sets  $req = 0$ .
- $C_2$  notices this, and concludes that the computation is finished: it sets  $ack = 0$  then waits for the next request.
- $C_1$  notices this, and proceeds to use  $r$  for whatever purpose it was computed.
- Since both  $req = 0$  and  $ack = 0$ , the process can now begin again from the start whenever  $C_1$  needs to perform another computation.

## A loop counter (2)

A control protocol

### Algorithm

 


#### Notes:

- Initially,  $req = 0$  and  $ack = 0$ .
- When  $C_1$  wants to compute something, it first drives any input values (say  $x$ ) then sets  $req = 1$  to signal they are ready for use.
- $C_2$  notices this, and starts computation. Eventually the computation is complete, meaning  $r = f(x)$ ; to signal this to  $C_1$ , it sets  $ack = 1$ .
- $C_1$  notices this, and concludes that the computation is finished: it latches  $r$ , and finally sets  $req = 0$ .
- $C_2$  notices this, and concludes that the computation is finished: it sets  $ack = 0$  then waits for the next request.
- $C_1$  notices this, and proceeds to use  $r$  for whatever purpose it was computed.
- Since both  $req = 0$  and  $ack = 0$ , the process can now begin again from the start whenever  $C_1$  needs to perform another computation.

## A loop counter (2)

A control protocol

### Algorithm

 


#### Notes:

- Initially,  $req = 0$  and  $ack = 0$ .
- When  $C_1$  wants to compute something, it first drives any input values (say  $x$ ) then sets  $req = 1$  to signal they are ready for use.
- $C_2$  notices this, and starts computation. Eventually the computation is complete, meaning  $r = f(x)$ ; to signal this to  $C_1$ , it sets  $ack = 1$ .
- $C_1$  notices this, and concludes that the computation is finished: it latches  $r$ , and finally sets  $req = 0$ .
- $C_2$  notices this, and concludes that the computation is finished: it sets  $ack = 0$  then waits for the next request.
- $C_1$  notices this, and proceeds to use  $r$  for whatever purpose it was computed.
- Since both  $req = 0$  and  $ack = 0$ , the process can now begin again from the start whenever  $C_1$  needs to perform another computation.

## A loop counter (2)

A control protocol

### Algorithm

 


#### Notes:

- Initially,  $req = 0$  and  $ack = 0$ .
- When  $C_1$  wants to compute something, it first drives any input values (say  $x$ ) then sets  $req = 1$  to signal they are ready for use.
- $C_2$  notices this, and starts computation. Eventually the computation is complete, meaning  $r = f(x)$ ; to signal this to  $C_1$ , it sets  $ack = 1$ .
- $C_1$  notices this, and concludes that the computation is finished: it latches  $r$ , and finally sets  $req = 0$ .
- $C_2$  notices this, and concludes that the computation is finished: it sets  $ack = 0$  then waits for the next request.
- $C_1$  notices this, and proceeds to use  $r$  for whatever purpose it was computed.
- Since both  $req = 0$  and  $ack = 0$ , the process can now begin again from the start whenever  $C_1$  needs to perform another computation.

## A loop counter (2)

A control protocol

### Algorithm

 


#### Notes:

- Initially,  $req = 0$  and  $ack = 0$ .
- When  $C_1$  wants to compute something, it first drives any input values (say  $x$ ) then sets  $req = 1$  to signal they are ready for use.
- $C_2$  notices this, and starts computation. Eventually the computation is complete, meaning  $r = f(x)$ ; to signal this to  $C_1$ , it sets  $ack = 1$ .
- $C_1$  notices this, and concludes that the computation is finished: it latches  $r$ , and finally sets  $req = 0$ .
- $C_2$  notices this, and concludes that the computation is finished: it sets  $ack = 0$  then waits for the next request.
- $C_1$  notices this, and proceeds to use  $r$  for whatever purpose it was computed.
- Since both  $req = 0$  and  $ack = 0$ , the process can now begin again from the start whenever  $C_1$  needs to perform another computation.

## A loop counter (2)

A control protocol


### Algorithm

 

#### Notes:

- Initially,  $req = 0$  and  $ack = 0$ .
- When  $C_1$  wants to compute something, it first drives any input values (say  $x$ ) then sets  $req = 1$  to signal they are ready for use.
- $C_2$  notices this, and starts computation. Eventually the computation is complete, meaning  $r = f(x)$ ; to signal this to  $C_1$ , it sets  $ack = 1$ .
- $C_1$  notices this, and concludes that the computation is finished: it latches  $r$ , and finally sets  $req = 0$ .
- $C_2$  notices this, and concludes that the computation is finished: it sets  $ack = 0$  then waits for the next request.
- $C_1$  notices this, and proceeds to use  $r$  for whatever purpose it was computed.
- Since both  $req = 0$  and  $ack = 0$ , the process can now begin again from the start whenever  $C_1$  needs to perform another computation.

A data-path

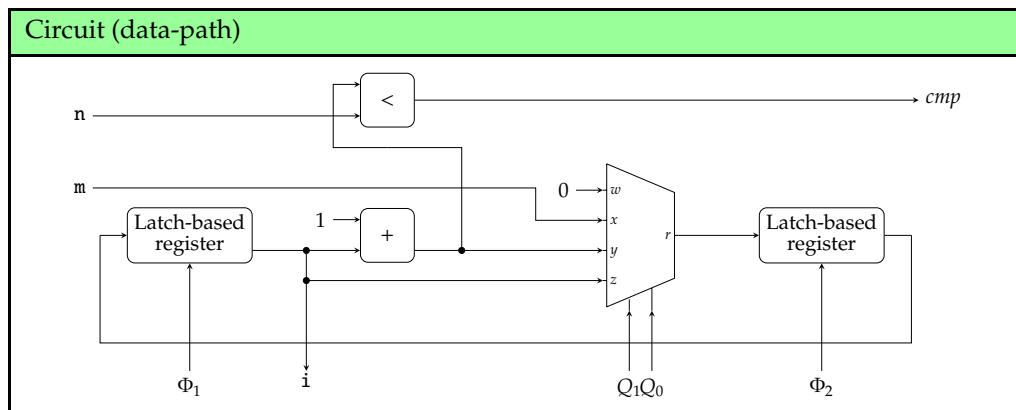

Notes:

- The general structure here is the same as the previous, uncontrolled counter example; the only difference is the the diagram is read from left-to-right rather than bottom-to-top. Otherwise, there is still
  1. an input register (a collection of D-type latches) enabled by  $\Phi_1$ ,
  2. some combinatorial logic that computes the next value of the counter from the current value, and
  3. an output register (a collection of D-type latches), enabled by  $\Phi_2$ .

When  $\Phi_2 = 1$  the output register is updated with whatever value is computed by the combinatorial logic: this is dictated by the  $Q$  input, acting as the multiplexer control signal. When  $\Phi_1 = 1$ , whatever was stored in the output register is fed back around and used to update the input register; after this, the cycle repeats.

A loop counter (4)

A control-path

- ▶ **Idea:** we can use an FSM to implement the control protocol.
- ▶ The FSM can be in one of 4 states, namely
  - ▶ in  $S_{wait}$  it waits for a request (i.e., for  $req = 1$ ),
  - ▶ in  $S_{init}$  it uses any input to initialise itself (e.g., setting the initial loop counter value),
  - ▶ in  $S_{step}$  it performs an iteration of the loop, and
  - ▶ in  $S_{done}$  it waits for  $req = 0$  (while setting  $ack = 1$ ) once the loop is complete.
- ▶ Since  $2^2 = 4$ , we can represent them using 4 concrete values, namely

$$\begin{array}{llll} S_{wait} & \mapsto & \langle 0, 0 \rangle & \equiv 00_{(2)} \\ S_{init} & \mapsto & \langle 1, 0 \rangle & \equiv 01_{(2)} \\ S_{step} & \mapsto & \langle 0, 1 \rangle & \equiv 10_{(2)} \\ S_{done} & \mapsto & \langle 1, 1 \rangle & \equiv 11_{(2)} \end{array}$$

and capture

1.  $Q = \langle Q_0, Q_1 \rangle \equiv$  the current state
2.  $Q' = \langle Q'_0, Q'_1 \rangle \equiv$  the next state

in a 2-bit register (i.e., via 2 latches or flip-flops).


Notes:

Algorithm (control-path, tabular)

		$\delta$		$\omega$	
$Q$		$Q'$		$ack$	
		$cmp = 0$	$cmp = 1$	$cmp = 0$	$cmp = 1$
$req = 0$	$S_{wait}$	$S_{wait}$	$S_{wait}$	0	0
	$S_{init}$	$S_{wait}$	$S_{wait}$	0	0
	$S_{step}$	$S_{wait}$	$S_{wait}$	0	0
	$S_{done}$	$S_{wait}$	$S_{wait}$	1	1
$req = 1$	$S_{wait}$	$S_{init}$	$S_{init}$	0	0
	$S_{init}$	$S_{step}$	$S_{step}$	0	0
	$S_{step}$	$S_{done}$	$S_{step}$	0	0
	$S_{done}$	$S_{done}$	$S_{done}$	1	1

Notes:

Algorithm (control-path, diagram)

 

Notes:

## Algorithm (control-path, truth table)


Rewriting the abstract labels yields the following concrete truth table:

				$\delta$		$\omega$
<i>req</i>	<i>cmp</i>	$Q_1$	$Q_0$	$Q'_1$	$Q'_0$	<i>ack</i>
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	0	1	1	0	0	1
0	1	0	0	0	0	0
0	1	0	1	0	0	0
0	1	1	0	0	0	0
0	1	1	1	0	0	1
1	0	0	0	0	1	0
1	0	0	1	1	0	0
1	0	1	0	1	1	0
1	0	1	1	1	1	1
1	1	0	0	0	1	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	1	1	1

Notes:
 
## Circuit (control-path, $\delta$ )

Translating the truth table into a set of Karnaugh maps



yields the following Boolean expressions:

$$Q'_1 = ( \text{req} \quad \quad \quad \wedge \quad Q_0 \quad ) \vee ( \text{req} \quad \quad \quad \wedge \quad Q_1 \quad )$$

$$Q'_0 = ( \text{req} \quad \quad \quad \wedge \quad \neg Q_1 \quad \wedge \quad \neg Q_0 \quad ) \vee ( \text{req} \quad \wedge \quad \quad \quad \wedge \quad Q_1 \quad \wedge \quad Q_0 \quad ) \vee ( \text{req} \quad \wedge \quad \neg \text{cmp} \quad \wedge \quad Q_1 \quad )$$

Notes:

## Circuit (control-path, $\omega$ )

Translating the truth table into a set of Karnaugh maps

			$Q_1$	
		$Q_0$		
$ack$				
	0	0	1	0
	0	0	1	0
$cmp$				
	0	0	1	0
	0	0	1	0
$req$				
	0	0	1	0

yields the following Boolean expressions:

$$ack = Q_1 \wedge Q_0$$


Notes:

## Conclusions

► **Next steps** (or, the lab. session):

1. We now have the loop counter implemented as specified, i.e.,

## Circuit (data- and control-paths)

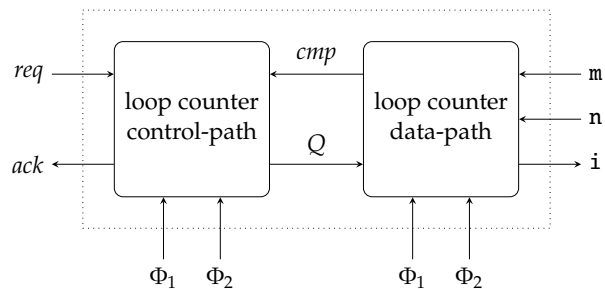


Notes:

- Now we understand how the FSM operates as a control path, we can be more specific about how the data path is controlled. Specifically, it should now be clear that
  1. if  $Q = (0, 0) \mapsto S_{init}$ , then the multiplexer updates the output register with 0,
  2. if  $Q = (1, 0) \mapsto S_{init}$  then the multiplexer updates the output register with  $m$ , i.e., the initial counter value,
  3. if  $Q = (0, 1) \mapsto S_{step}$  then the multiplexer updates the output register with  $i + 1$ , i.e., the incremented counter value produced by the adder,
  4. if  $Q = (1, 1) \mapsto S_{done}$  then the multiplexer updates the output register with  $i$ , i.e., the current counter value.

## Conclusions

### ► Next steps (or, the lab. session):

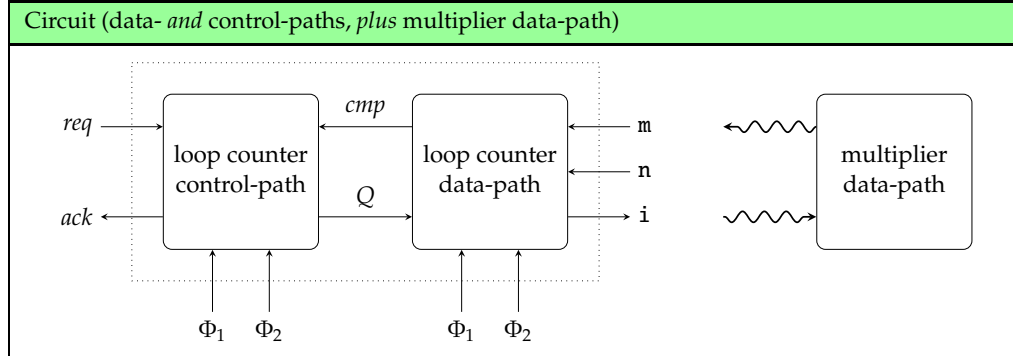1. We now have the loop counter implemented as specified, i.e.,



2. The next challenge is then *using* it to realise the original goal, e.g., specifying

- any additional data-path components required, and
- how loop counter (the control-path) controls them

so we end up with a bit-serial multiplier.

Notes:

- Now we understand how the FSM operates as a control path, we can be more specific about how the data path is controlled. Specifically, it should now be clear that
  1. if  $Q = \langle 0, 0 \rangle \mapsto S_{init}$ , then the multiplexer updates the output register with 0,
  2. if  $Q = \langle 1, 0 \rangle \mapsto S_{init}$  then the multiplexer updates the output register with  $m$ , i.e., the initial counter value,
  3. if  $Q = \langle 0, 1 \rangle \mapsto S_{add}$  then the multiplexer updates the output register with  $i + 1$ , i.e., the incremented counter value produced by the adder,
  4. if  $Q = \langle 1, 1 \rangle \mapsto S_{done}$  then the multiplexer updates the output register with  $i$ , i.e., the current counter value.

## Additional Reading

- *Wikipedia: Computer Arithmetic*. URL: [http://en.wikipedia.org/wiki/Category:Computer\\_arithmetic](http://en.wikipedia.org/wiki/Category:Computer_arithmetic).
- D. Page. "Chapter 7: Arithmetic and logic". In: *A Practical Introduction to Computer Architecture*. 1st ed. Springer-Verlag, 2009.
- B. Parhami. "Part 3: Multiplication". In: *Computer Arithmetic: Algorithms and Hardware Designs*. 1st ed. Oxford University Press, 2000.
- W. Stallings. "Chapter 10: Computer arithmetic". In: *Computer Organisation and Architecture*. 9th ed. Prentice-Hall, 2013.
- A.S. Tanenbaum and T. Austin. "Section 3.2.2: Arithmetic circuits". In: *Structured Computer Organisation*. 6th ed. Prentice-Hall, 2012.

Notes:



## References

- [1] [Wikipedia: Computer Arithmetic](http://en.wikipedia.org/wiki/Category:Computer_arithmetic). URL: [http://en.wikipedia.org/wiki/Category:Computer\\_arithmetic](http://en.wikipedia.org/wiki/Category:Computer_arithmetic) (see p. 63).
- [2] D. Page. “Chapter 7: Arithmetic and logic”. In: *A Practical Introduction to Computer Architecture*. 1st ed. Springer-Verlag, 2009 (see p. 63).
- [3] B. Parhami. “Part 3: Multiplication”. In: *Computer Arithmetic: Algorithms and Hardware Designs*. 1st ed. Oxford University Press, 2000 (see p. 63).
- [4] W. Stallings. “Chapter 10: Computer arithmetic”. In: *Computer Organisation and Architecture*. 9th ed. Prentice-Hall, 2013 (see p. 63).
- [5] A.S. Tanenbaum and T. Austin. “Section 3.2.2: Arithmetic circuits”. In: *Structured Computer Organisation*. 6th ed. Prentice-Hall, 2012 (see p. 63).

Notes: